

Design of 4:1 Multiplexer using CMOS Logic

Gaeya Sri Satya Vinnakota, BTech, Electronics Engineering, Sardar Vallabhbhai National Institute of Technology
19 February 2022

Abstract

This report describes the design and implementation of 4:1 Multiplexer using CMOS logic using the Cloud-based Synopsys tool at the 28nm CMOS technology node. Multiplexer circuit selects 1 output data line from multiple input data lines with the help of input select lines. This design discussed in the report uses 4 input data lines and 2 input select lines to get the 1 output data line.

1.REFERENCE CIRCUIT DETAILS

A Multiplexer circuit, shortly called MUX, is used to select a data line as output from multiple input data lines by using input select lines. To get an output data line from N input data lines that is N:1 MUX, we require \log_2^N select lines.

The representation of 4:1 MUX is shown in Figure-1, and the truth table of the 4:1 MUX is shown in Figure-2.

 


Figure 1 - Representation of 4:1 MUX

S_0	S_1	Out
0	0	A
1	0	B
0	1	C
1	1	D

Figure 2 - Truth Table of 4:1 MUX

In this report, a 4:1 MUX is designed using CMOS logic (Figure-3). Here both the Pull-up (made of the PMOS) and pull-down (made of the NMOS) networks pull the output to the input data lines, and the input select lines are given to the MOSFETs' gates.

2.REFERENCE CIRCUIT

 


Figure 3 - Reference Circuit

3.REFERENCE WAVEFORMS

 


Figure 4 - Reference Waveforms

REFERENCES

- [1] <https://en.wikipedia.org/wiki/Multiplexer>
- [2] https://www.electronics-tutorials.ws/combinational/comb_2.html
- [3] <https://www.electronics-tutorial.net/Digital-CMOS-Design/Pass-Transistor-Logic/4-1-multiplexer-using-CMOS-logic/>